

**Ve270 Introduction to Logic Design**

**Homework 10**

**Assigned: November 28, 2019**

**Due: December 5, 2019, 4:00pm.**

**The homework should be submitted in hard copies.**

1. Problem 5.25 (20 points)


(a) Assume the 8-bit carry-ripple adder consists of 8 full-adders chained together. Each full-adder features a critical path delay of 4ns (an AND gate and a XOR gate). Thus, the total critical path delay for the 8-bit carry-ripple adder is  $8 \times 4\text{ns} = 32\text{ns}$ .

(b) Each full-adder's critical path features one internal wire between an AND and XOR gate and two wires that connect the full-adder's inputs and outputs. For the entire 8-bit carry-ripple adder, the 8 internal wires contribute 8ns to the critical path delay. Wires connecting full-adders together contribute 7ns to the critical path delay.

The initial ci and final co contribute 2ns to the critical path delay. Thus, the total critical path delay is  $32\text{ns}$  (for gates) +  $8\text{ns}$  +  $7\text{ns}$  +  $2\text{ns} = 49\text{ns}$ .

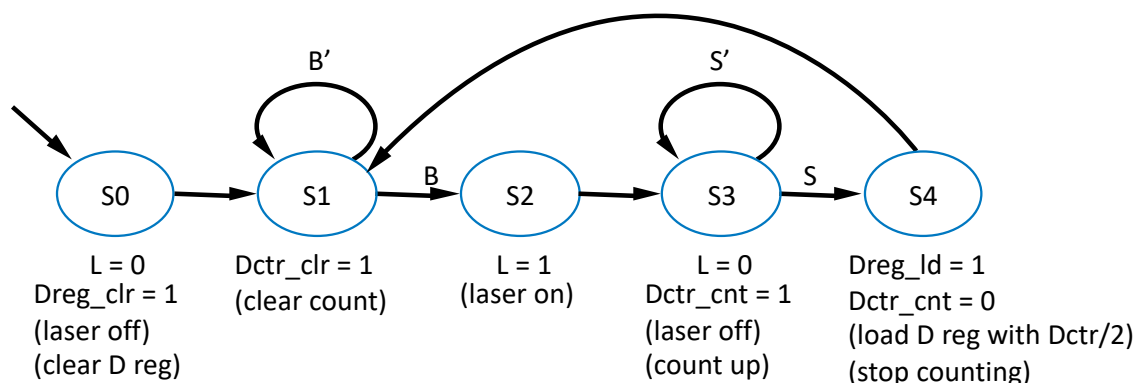2. Problem 5.26 (30 points)

Inputs: B, S      Outputs: L, Dreg\_clr, Dreg\_ld, Dctr\_clr, Dctr\_cnt



(a)

Inputs					Outputs							
s2	s1	s0	B	S	n2	n1	n0	L	Dreg_clr	Dreg_ld	Dctr_clr	Dctr_cnt
0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	1	0	0	1	0	1	0	0	0
0	0	0	1	0	0	0	1	0	1	0	0	0
0	0	0	1	1	0	0	1	0	1	0	0	0
0	0	1	0	0	0	0	1	0	0	0	1	0
0	0	1	0	1	0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0	0	0	0	1	0
0	0	1	1	1	0	1	0	0	0	0	1	0
0	1	0	0	0	0	1	1	1	0	0	0	0
0	1	0	0	1	0	1	1	1	0	0	0	0
0	1	0	1	0	0	1	1	1	0	0	0	0
0	1	0	1	1	0	1	1	1	0	0	0	0
0	1	1	0	0	0	1	1	0	0	0	0	1
0	1	1	0	1	1	0	0	0	0	0	0	1
0	1	1	1	0	0	1	1	0	0	0	0	1
0	1	1	1	1	1	0	0	0	0	0	0	1
1	0	0	0	0	0	0	1	0	0	1	0	0
1	0	0	0	1	0	0	1	0	0	1	0	0
1	0	0	1	0	0	0	1	0	0	1	0	0
1	0	0	1	1	0	0	1	0	0	1	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0
1	0	1	1	1	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0
1	1	0	1	1	0	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0	0	0
1	1	1	0	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0

$$n2 = s1's1s0B'S + s2's1s0BS$$

$$n1 = s2's1's0B + s2's1s0' + s2's1s0S'$$


$$n0 = s2's1's0' + s2's1's0B' + s2's1s0' + s2's1s0S' + s2s1's0'$$

$$Dreg\_clr = s2's1's0'$$

$$Dreg\_ld = s2s1's0'$$

$$Dctr\_clr = s2's1's0$$

$$\text{Dctr\_ctr} = s2's1s0$$

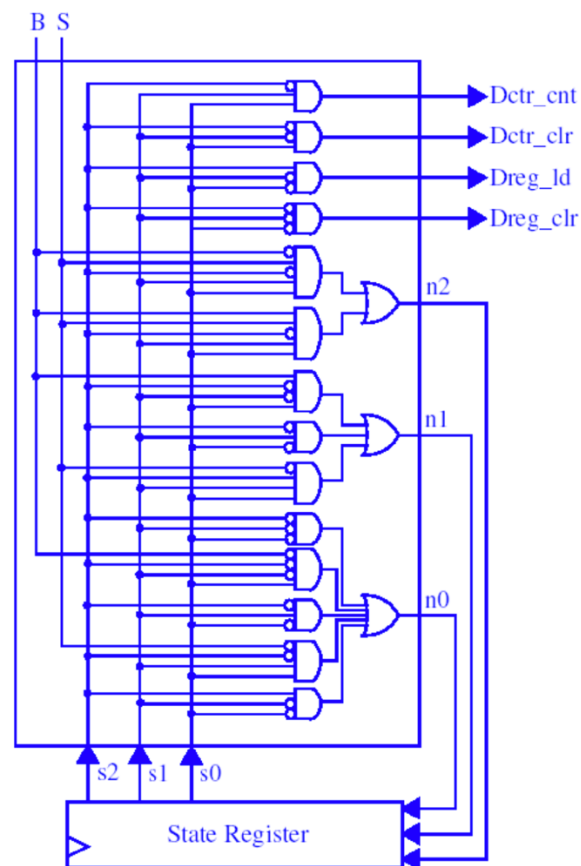

(b) The controller features two levels of gates, resulting in a delay of 4ns. Therefore the critical path is within the up-counter, or 5ns.

(c) With a critical path of 5ns, the maximum clock frequency is  $1,000,000,000/5 = 200\text{MHz}$ .

3. Given that an SRAM block has a 32-bit address input, each line of the memory has an address, how many lines does the memory have? (5 points)

The SRAM block has  $2^{32}$  lines

If each line is a 32-bit word, how many bytes (8 bits) does the memory have? (2 points)

It has  $2^{32} * 4 = 2^{34}$  bytes

In that case, how many transistors does the memory have for storage? (3 points)

Each bit is stored in one SRAM cell which requires 6 transistors.

$2^{34}$  bytes =  $2^{34} * 8$  bits =  $2^{37}$  bits

Number of transistors =  $2^{37} * 6$

If we use a decoder to decode the address, how big a decoder will be needed (e.g. a 3x8 decoder)? (2 points)

32 x  $2^{32}$  decoder


If the memory is byte addressable, i.e. each byte has an address, how many bits does the memory have? (3 points)

With 32 bits of address, we have  $2^{32}$  addresses. If the addresses are for bytes, then we have  $2^{32}$  bytes. Then number of bits =  $2^{32} * 8 \text{ bits} = 2^{35} \text{ bits}$ .

4. Use one 4-input LUT to implement the following Boolean function (15 points)

$$f = x_2x_3'x_4' + x_1'x_2x_4 + x_1'x_2x_3 + x_1x_2x_3$$

x1	x2	x3	x4	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

 

### 5. Problem 7.20 (20 points)

